


Using a multimeter

The practical work supporting Chapter 15 introduces you to using a multimeter to make measurements from circuits. Once you are able to test circuits, you will understand better how they work and be able to locate and correct faults.

What do meters measure?

A meter is a measuring instrument. An **ammeter** measures current, a **voltmeter** measures the potential difference (voltage) between two points, and an **ohmmeter** measures resistance. A **multimeter** combines these functions, and possibly some additional ones as well, into a single instrument.

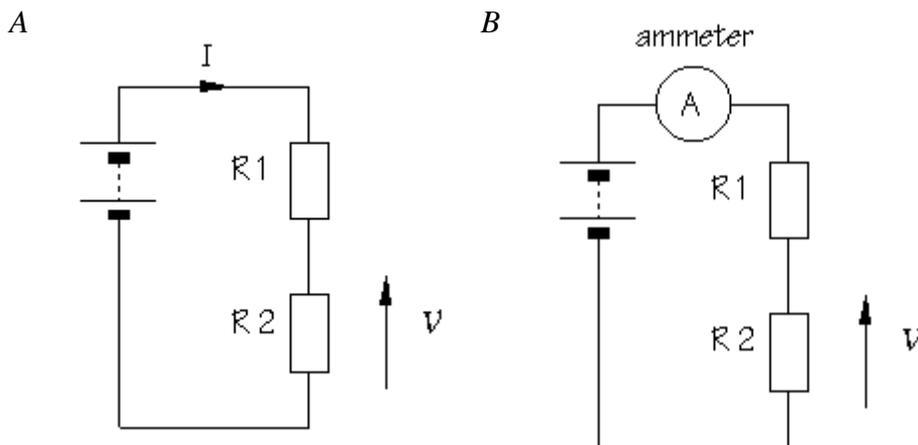Before going in to detail about multimeters, it is important for you to have a clear idea of how meters are connected into circuits. Diagrams *A* and *B* below show a circuit before and after connecting an ammeter:





to measure current, the circuit must be broken to allow the ammeter to be connected in series

ammeters must have a LOW resistance

Think about the changes you would have to make to a practical circuit in order to include the ammeter. To start with, you need to *break the circuit* so that the ammeter can be connected in series. All the current flowing in the circuit must pass through the ammeter. Meters are not supposed to alter the behavior of the circuit, or at least not significantly, and it follows that an ammeter must have a very LOW resistance.

Diagram *C* shows the same circuit after connecting a voltmeter:

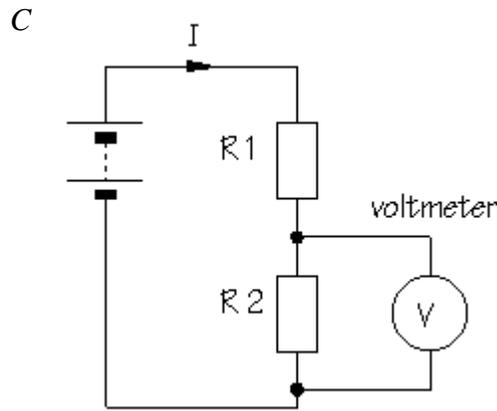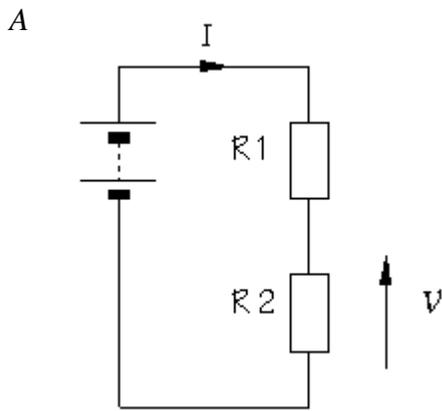

**to measure potential difference (voltage), the circuit is not changed:
the voltmeter is connected in parallel**



voltmeters must have a HIGH resistance

This time, you do not need to break the circuit. The voltmeter is connected in parallel between the two points where the measurement is to be made. Since the voltmeter provides a parallel pathway, it should take as little current as possible. In other words, a voltmeter should have a very HIGH resistance.

Which measurement technique do you think will be the more useful? In fact, voltage measurements are used much more often than current measurements.

The processing of electronic signals is usually thought of in voltage terms. It is an added advantage that a voltage measurement is easier to make. The original circuit does not need to be changed. Often, the meter probes are connected simply by touching them to the points of interest.

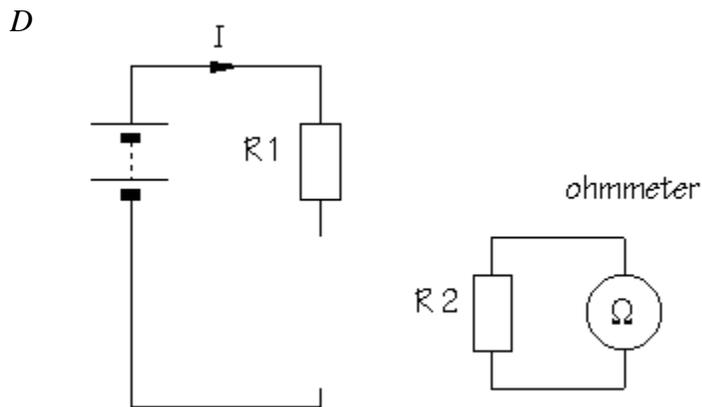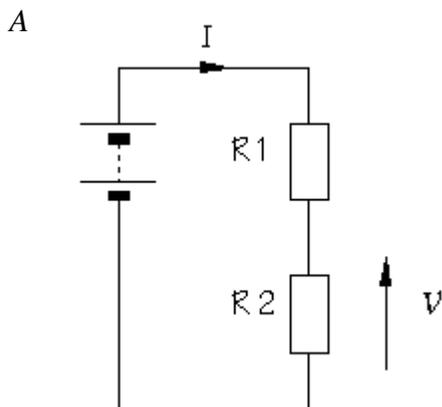An ohmmeter does not function with a circuit connected to a power supply. If you want to measure the resistance of a particular component, you must take it out of the circuit altogether and test it separately, as shown in diagram D:



to measure resistance, the component must be removed from the circuit altogether


ohmmeters work by passing a current through the component being tested

Ohmmeters work by passing a small current through the component and measuring the voltage produced. If you try this with the component connected into a circuit with a power supply, the most likely result is that the meter will be damaged. Most multimeters have a fuse to help protect against misuse.

Digital multimeters (DMM)

Multimeters are designed and mass produced for electronics engineers. Even the simplest and cheapest types may include features which you are not likely to use. Digital meters give an output in numbers, usually on a liquid crystal display.

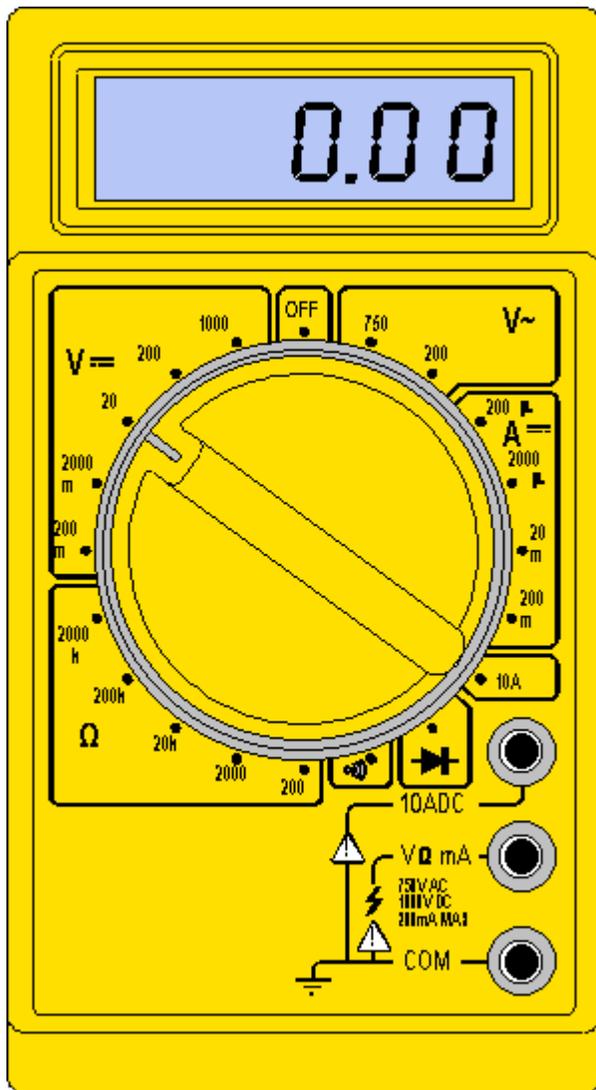The diagram below shows a **switched range multimeter**:



← Switched range multimeter

The central knob has lots of positions and you must choose which one is appropriate for the measurement you want to make. If the meter is switched to 20 V DC, for example, then 20 V is the maximum voltage which can be measured. This is sometimes called 20 V **fsd**, where fsd is short for **full scale deflection**.

For circuits with power supplies of up to 20 V, which includes all the circuits you are likely to build, the 20 V DC voltage range is the most useful. DC ranges are indicated by **V=** on the meter. Sometimes, you will want to measure smaller voltages, and in this case, the 2 V or 200 mV ranges are used.

What does DC mean? DC means **direct current**. In any circuit which operates from a steady voltage source, such as a battery, current flow is always in the same direction. Every constructional project described in this class works in this way.


AC means **alternating current**. In an electric lamp connected to the domestic mains electricity, current flows first one way, then the other. That is, the current reverses, or alternates, in direction. In the US, the current reverses 60 times per second.

⚠ MAINS VOLTAGE ⚠

For safety reasons, you must NEVER connect a multimeter to the mains supply.

You are not at all likely to use the AC ranges, indicated by **V~**, on your multimeter.

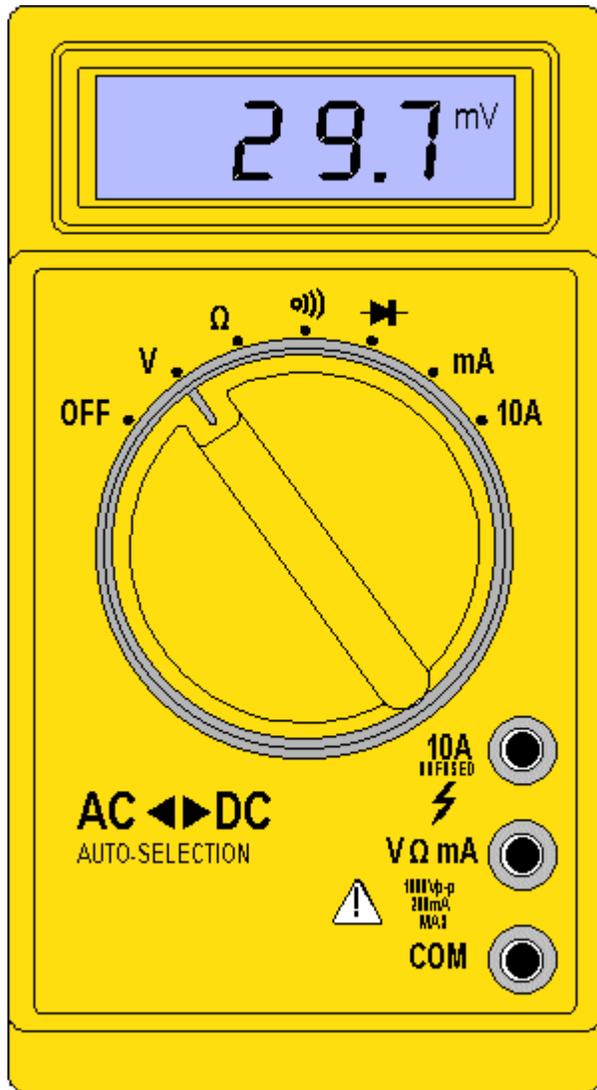An alternative style of multimeter is the **autoranging multimeter**:



← *Autoranging multimeter*

The central knob has fewer positions and all you need to do is to switch it to the quantity you want to measure. Once switched to V, the meter automatically adjusts its range to give a meaningful reading, and the display includes the unit of measurement, V or mV. This type of meter is more expensive, but obviously much easier to use.

Where are the two meter probes connected? The **black** lead is always connected into the socket marked COM, short for COMMON. The **red** lead is connected into the socket labelled V Ω mA. The 10A socket is very rarely used.